

1. (i) Design a Half-subtractor (HS) using Half-Adder (HA).
(ii) Design a Full-Adder (FA) using Full-Subtractor (FS)
You may use inverters as per your requirement.
2. Design a 1-bit comparator that takes in a bit X and a bit Y and outputs $X < Y$, $X > Y$, $X = Y$.
Use a single 2-to-4 decoder and 1 single OR gate.
3. Design the sum output of a Full Adder using only two 4:1 multiplexers.
4. Design a 3-bit Binary to Gray converter using only one 3:8 decoder and one 8:3 encoder.
5. Implement the following function (SOP) using 2:4 decoders and OR gate only.

$$F(W, X, Y, Z) = \sum (1, 4, 7, 9, 10)$$

6. Implement following function using 8:1 MUX.

$$F(A, B, C, D) = \sum (0, 1, 2, 3, 4, 9, 13, 14, 15)$$