

Ques 1: Given a Boolean function

$$f(a, b, c, d) = \sum m(0, 1, 5, 7, 11, 14) + d(12, 15)$$

Implement the function with a minimal network of 2:1 multiplexer. Consider that true and false forms of inputs are available.

$$f(a, b, c, d) = \sum m(0, 1, 5, 7, 11, 14) + d(12, 15)$$


		cd			
		00	01	11	10
ab	00	1	1	0	0
	01	0	1	1	0
	11	X	0	X	1
	10	0	0	1	0

$\bar{a}\bar{b}\bar{c}$ ← (points to cell 00, 00)
 ← (points to cell 01, 01) $\bar{a}bd$
 $ab\bar{d}$ ← (points to cell 11, 11)
 ← (points to cell 11, 10) acd


$$f(a, b, c, d) = \bar{a}\bar{b}\bar{c} + \bar{a}bd + ab\bar{d} + acd$$


$$f = \bar{a}\bar{b}\bar{c} + \bar{a}bd + ab\bar{d} + acd$$
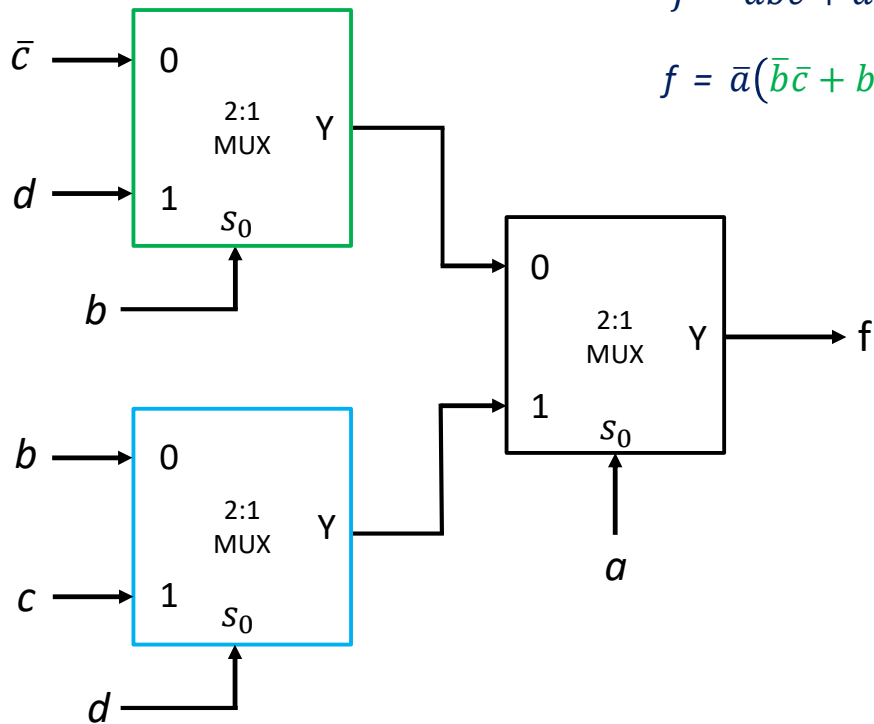
$$f = \bar{a}(\bar{b}\bar{c} + bd) + a(b\bar{d} + cd)$$



 Ques 2: For the sequential circuit shown below, t_{pd} is the propagation delay, t_{setup} is the setup time, and t_{hold} is the hold time. Find the maximum clock frequency at which this circuit can operate reliably.



 

Setup Time: It is the amount of time for which the data at the synchronous input must be stable before the active edge of the clock.

Hold Time: It is the amount of time for which the data of the synchronous input must be stable after the active edge of the clock.

Maximum clock frequency = The minimum time after which the next clock edge arrives

For Flip-Flop 1:

After the arrival of a clock edge, the output becomes stable after $t_{pd} = 8 \text{ ns}$.

The output is then passed through on XOR gate and a NAND gate.

The net delay will be: $3\text{ns} + 2\text{ns} + 2\text{ns} = 7\text{ns}$

This output from the NAND gate after 7 nsec must remain stable for at least t_{setup} time of FF2

So, the minimum time after which the next clock edge should arrive at FF 1 is

$$(T_{\min})_{\text{FF1}} = 7 \text{ ns} + 4\text{ns} = \mathbf{11 \text{ ns}}$$

For Flip-Flop 2:

After the arrival of a clock edge, the output becomes stable after $t_{\text{hold}} = 3 \text{ ns}$.

The output of FF2 is the input to FF1, this output after $t_{\text{pd}} = 8 \text{ ns}$ must remain stable for at least (t_{setup}) time of FF1, i.e.. for 5 ns, before the next clock edge should arrive at FF1.

The minimum time after which the next clock should arrive at FF1 should be:

$$(T_{\text{min}})_{\text{FF2}} = 8 \text{ ns} + 5 \text{ ns} = \mathbf{13 \text{ ns}}$$

For the given circuit to operate reliably, the minimum clock time


$$(T_{\min})_{\text{CLK}} = \max[(T_{\min})_{\text{FF1}} , (T_{\min})_{\text{FF2}}] = 13 \text{ ns}$$


The maximum clock frequency will be

$$(f_{\text{clk}})_{\max} = \frac{1}{(T_{\min})_{\text{CLK}}}$$

$$(f_{\text{clk}})_{\max} = \frac{1}{13 \text{ ns}} = \mathbf{76.92 \text{ MHz}}$$

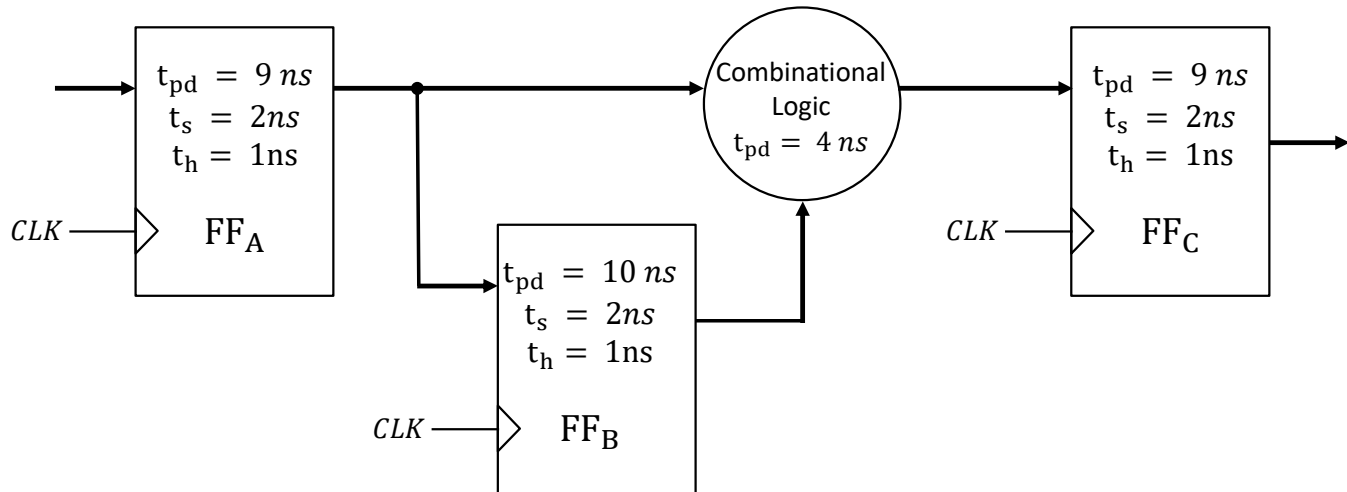Ques 3: For the sequential circuit shown below, t_{pd} is the propagation delay, t_{setup} is the setup time, and t_{hold} is the hold time. Find the maximum clock frequency at which this circuit can operate reliably.



 

Setup Time: It is the amount of time for which the data at the synchronous input must be stable before the active edge of the clock.

Hold Time: It is the amount of time for which the data of the synchronous input must be stable after the active edge of the clock.

Input is applied at FF_A and output is obtained at FF_C.

Two possible routes from input to output:

1. FF_A \longrightarrow Comb. logic \longrightarrow FF_C

Minimum time required for stable output at FF_C :

$$9 \text{ ns} + 4 \text{ ns} + 2 \text{ ns} = 15 \text{ ns}$$

2. FF_A \longrightarrow FF_B \longrightarrow Comb. logic \longrightarrow FF_C

Minimum time required for stable output at FF_C :

$$10 \text{ ns} + 4 \text{ ns} + 2 \text{ ns} = 16 \text{ ns}$$

$$(T_{\min})_{\text{CLK}} = \max[(T_{\min})_{\text{FF1}} , (T_{\min})_{\text{FF2}}] = 16 \text{ ns}$$

The maximum clock frequency will be

$$(f_{\text{clk}})_{\max} = \frac{1}{(T_{\min})_{\text{CLK}}}$$

$$(f_{\text{clk}})_{\max} = \frac{1}{16 \text{ ns}} = \mathbf{62.5 \text{ MHz}}$$

Ques 4: Transform the S-R flip flop to

- a) T flip flop
- b) J-K flip flop
- c) D flip flop

Characteristics equation of SR Flip-flop: $S + \bar{R} Q_n = Q_{n+1}$ (applied S.R = 0)

Characteristics equation of T Flip-flop: $T + Q_n = Q_{n+1}$

Characteristics equation of JK Flip-flop: $J \bar{Q}_n + \bar{K} Q_n = Q_{n+1}$


Characteristics equation of D Flip-flop: $D = Q_{n+1}$

Transforming SR Flip-flop to T Flip-flop

Characteristic Table of T Flip-flop			Excitation Table of SR Flip-flop	
T	Q_n	Q_{n+1}	S	R
0	0	0	0	X
0	1	1	X	0
1	0	1	1	0
1	1	0	0	1

Solving K-map for S and R separately with T and Q_n as inputs, we get:
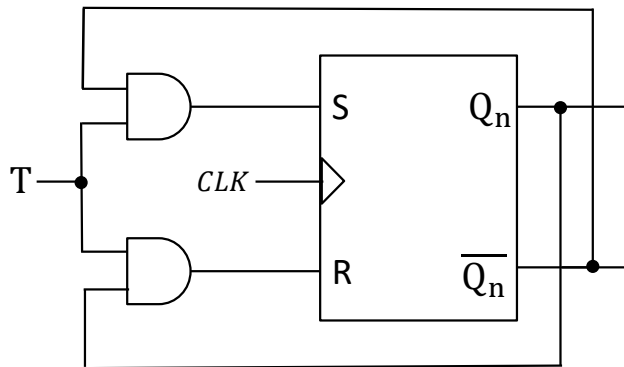
$$S = T \overline{Q_n} \text{ and } R = T Q_n$$




Transforming SR Flip-flop to D Flip-flop

Characteristic Table of D Flip-flop			Excitation Table of SR Flip-flop	
D	Q_n	Q_{n+1}	S	R
0	0	0	0	X
0	1	0	0	1
1	0	1	1	0
1	1	1	X	0

Solving K-map for S and R separately with D and Q_n as inputs, we get:

$$S = D \text{ and } R = \bar{D}$$

 

Transforming SR Flip-flop to JK Flip-flop

Characteristic Table of JK Flip-flop				Excitation Table of SR Flip-flop	
J	K	Q_n	Q_{n+1}	S	R
0	0	0	0	0	X
0	0	1	1	X	0
0	1	0	0	0	X
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	1	X	0
1	1	0	1	1	0
1	1	1	0	0	1

Solving K-map for S and R separately with D and Q_n as inputs, we get:

$$S = J \overline{Q_n} \text{ and } R = K Q_n$$

